
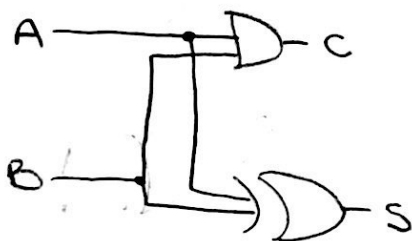


Circuit Demonstration Page

Half adder schematic

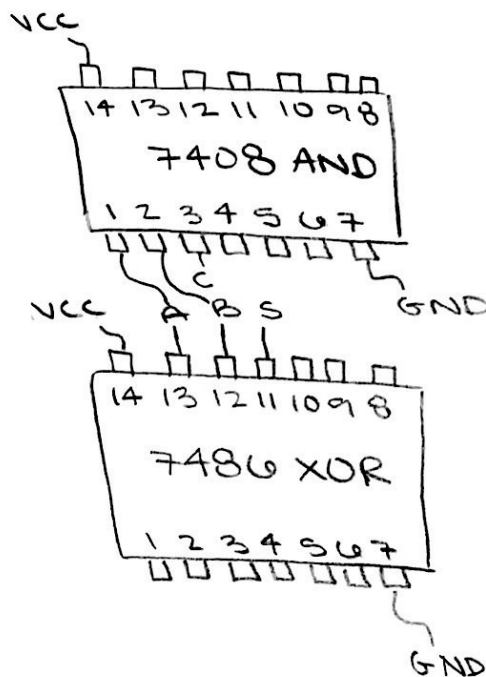


Half adder wiring diagram




Half adder: BD

Full adder schematic

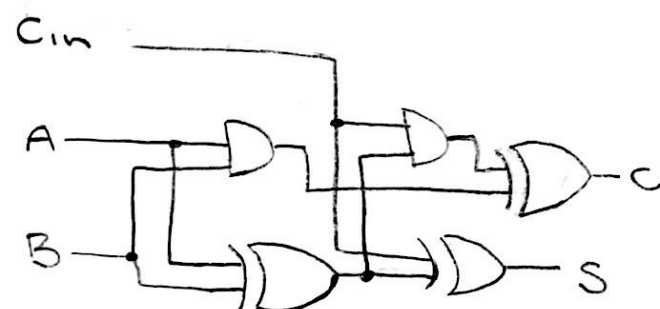

Full adder wiring diagram

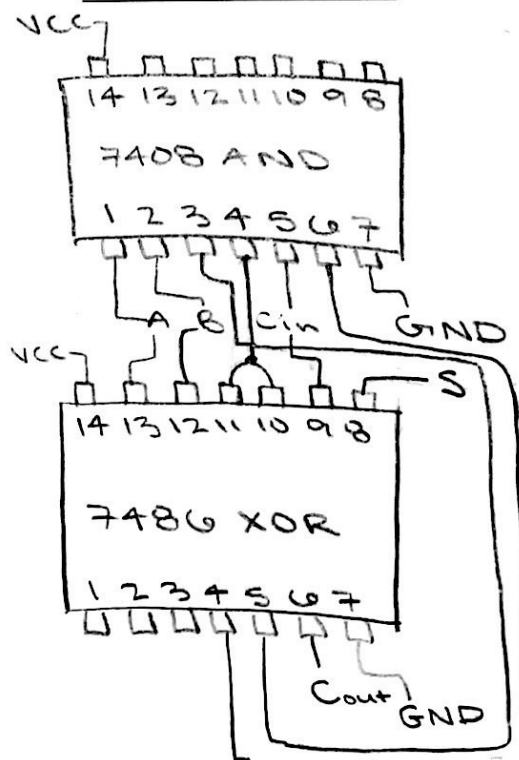

Full adder: BD

2-bit adder: BD