

# ELC 2137 Lab 5: Intro to Verilog

Trevor Jackson, Carlos Hernandez, and Makenna Meyers

February 17, 2020

## Summary

This lab was an introduction to coding with Verilog. We learned to code the half adder, full adder, and adder/subtractor circuits that we had assembled with wires in previous labs. The codes for the adders and their test benches can be found below in Codes [1](#), [2](#), [3](#), [4](#), [5](#), and [6](#). Expected Results Tables (ERTs) and simulation waveforms for each adder can be found in Figures [1](#), [2](#), and [3](#). In addition to writing and testing the code for the adders, block diagrams were drawn to illustrate the inputs, outputs, wires, and gates involved with each circuit. Those can be found in Figures [4](#), [5](#), and [6](#).

## Q&A

1. What is one thing you still don't understand about Verilog?

What is the most efficient way to implement the logic gates?

## Results

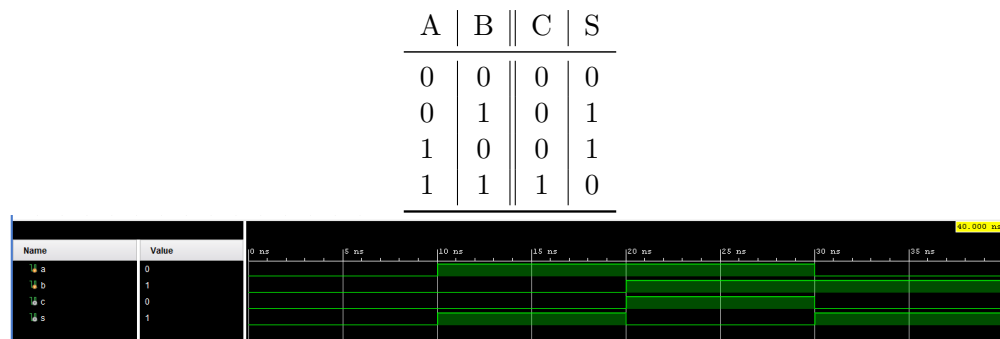


Figure 1: Half Adder ERT and Simulation Waveform

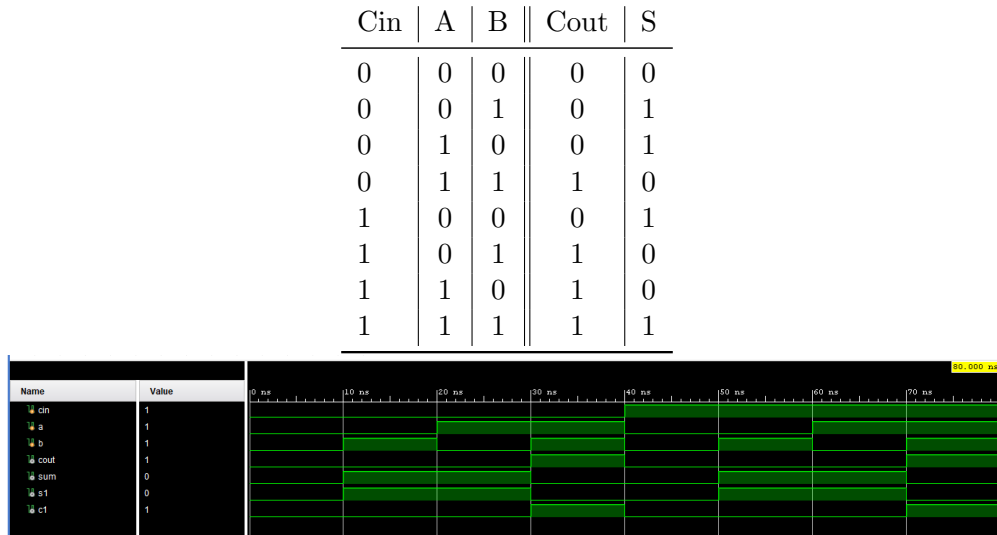


Figure 2: Full Adder ERT and Simulation Waveform

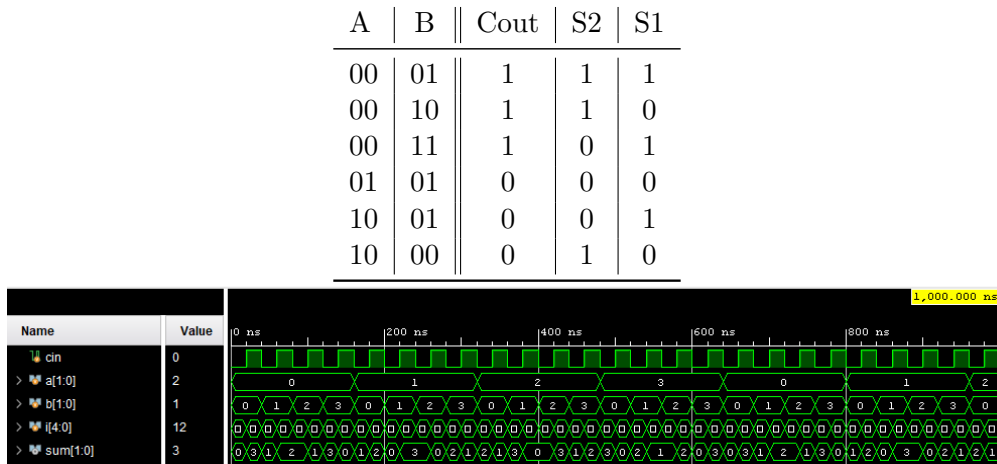


Figure 3: Adder/Subtractor ERT and Simulation Waveform

 


Figure 4: Half Adder Block Diagram

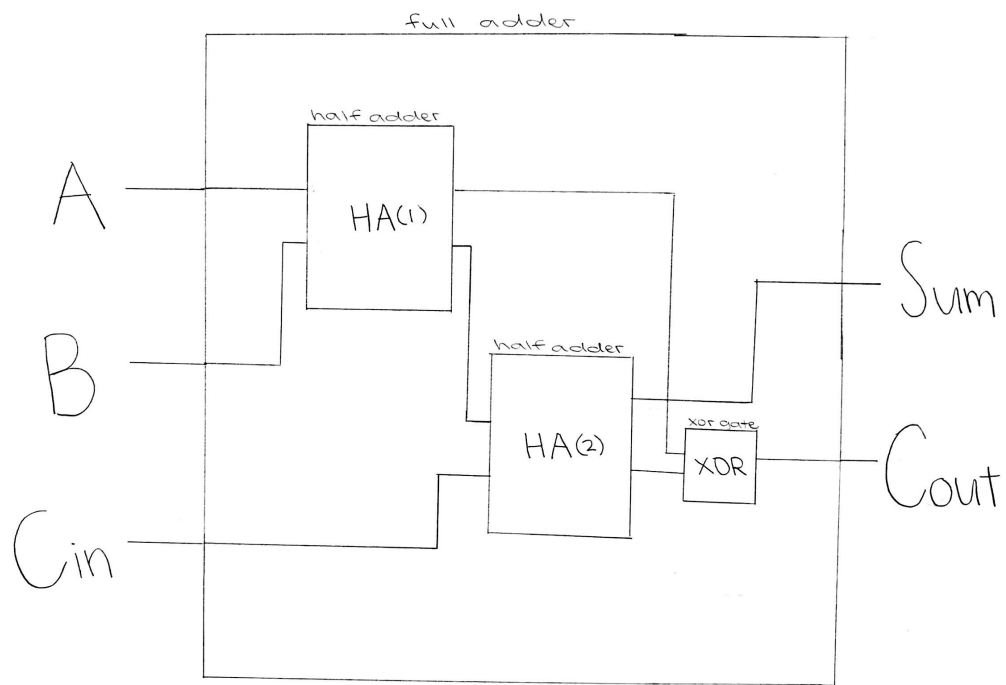


Figure 5: Full Adder Block Diagram

 


Figure 6: Adder/Subtractor Block Diagram

## Code

### Listing 1: Half Adder Code

```
'timescale 1ns / 1ps
//
// //////////////////////////////////////
// Company:
// Engineer:
//
// Create Date: 02/11/2020 02:33:52 PM
// Design Name:
// Module Name: halfadder
// Project Name:
// Target Devices:
// Tool Versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
//
// //////////////////////////////////////

module halfadder (input a, b,output s, c);
assign s = a ^ b;
assign c = a & b;

endmodule
```

Listing 2: Half Adder Test Bench Code

```
'timescale 1ns / 1ps

module  halfadder_test ();
    reg a, b;
    wire c, s;

    halfadder  ha0(
        .a(a), .b(b),
        .c(c), .s(s)
    );

    initial  begin
        a=0; b=0;  #10;
        a=1; b=0;  #10;
        a=1; b=1;  #10;
        a=0; b=1;  #10;
    end
endmodule
```

```
        $finish;
    end
endmodule
```

Listing 3: Full Adder Code

```
timescale 1ns / 1ps
//
// Company:
// Engineer:
//
// Create Date: 02/11/2020 03:26:50 PM
// Design Name:
// Module Name: fulladder
// Project Name:
// Target Devices:
// Tool Versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
//
//
module fulladder (input a, b, cin ,output sum , cout);

wire s1 , c1, c2;
halfadder ha0(.a(a), .b(b), .s(s1), .c(c1));
halfadder ha1(.a(a), .b(b), .s(sum), .c(cout));

or o1(cout,c1,c2);
/*assign c1 = a&b;
assign s1 = a^b;
assign c2 = cin & s1;

assign sum = cin & s1;
assign cout = c1 | c2; */
endmodule
```

Listing 4: Full Adder Test Bench Code

```
'timescale 1ns / 1ps

module  fulladder_test ();
reg cin;
reg [3:0] a , b;
```

```

wire  cout , sum;

halfadder  ha0(.a(a), .b(b), .s(s1), .c(c1));
initial begin
    cin=0; a=0; b=0;  #10;
    cin=0; a=0; b=1;  #10;
    cin=0; a=1; b=0;  #10;
    cin=0; a=1; b=1;  #10;
    cin=1; a=0; b=0;  #10;
    cin=1; a=0; b=1;  #10;
    cin=1; a=1; b=0;  #10;
    cin=1; a=1; b=1;  #10;

    $finish;
end

halfadder  ha1(.a(a), .b(b), .s(sum), .c(cout));
initial begin
    cin=0; a=0; b=0;  #10;
    cin=0; a=0; b=1;  #10;
    cin=0; a=1; b=0;  #10;
    cin=0; a=1; b=1;  #10;
    cin=1; a=0; b=0;  #10;
    cin=1; a=0; b=1;  #10;
    cin=1; a=1; b=0;  #10;
    cin=1; a=1; b=1;  #10;

    $finish;
end
endmodule

```

---

Listing 5: Adder/Subtractor Code

---

```

`timescale 1ns / 1ps

module addersub(input cin,
                input [1:0] a, b,
                output cout, V,
                output [1:0] sum);

    wire x0,x1;
    wire c0;

    xor (x0, b[0], cin);
    xor (x1, b[1], cin);
    xor (cout, c1, cin);
    xor (V, c1, c0);

    fulladder fa0(.a(a[0]), .b(x0), .cin(cin), .sum(sum[0]), .cout(c0)
    );
    fulladder fa1(.a(a[1]), .b(x1), .cin(c0), .sum(sum[1]), .cout(c1))
    ;

```

```
endmodule
```

---

### Listing 6: Adder/Subtractor Test Bench Code

---

```
'timescale 1ns / 1ps

module addersub_test();
    reg cin;
    reg [1:0] a, b;
    reg [4:0] i;
    wire [1:0] sum;
    wire cout;

    addersub AS(.a(a), .b(b), .cin(cin), .sum(sum), .cout(cout));

    initial
        begin
            for(i=0; i <= 8'hff; i = i+1)
                begin
                    a[1:0] = i [4:3];
                    b[1:0] = i [2:1];
                    cin = i[0];
                    #20;
                end
            end
        end
endmodule
```

---